 


Cadence Full-Custom IC Design

Ph. D. ByoungJin Lee



CONTENTS



Step 1.

Introduction



Step 3.

Analog Circuit
(CS / DIFF AMP)




Step 2.

Digital Circuit
(Logic Gate / MUX / Adder)




Step 4.

Summary

 



1. INTRODUCTION

 

❖ Course

Nineplus IT - Cadence® Full-Custom IC Designer



❖ Tools


Cadence Virtuoso Schematic Editor / Layout Editor

Cadence Virtuoso Spectre / ADE

Assura DRC / LVS




GPDK090

 

2. DIGITAL CIRCUIT


Logic Gate	Multiplexer (MUX)	Adder
NOT (Inverter)	2X1 MUX (Gate / Switch)	Half Adder
Switch (Transmission Gate)	4X1 MUX (Gate / Switch)	Full Adder
2~4 NAND / NOR	-	4-bit Adder

 


2-1. LOGIC GATE

- ❖ Find the width of PMOS – NOT GATE

①

 



②

 

2-1. LOGIC GATE

- ❖ Find the width of PMOS – NOT GATE



③

  

2-1. LOGIC GATE



□ Mosfet Width (Length = 100nm)

❖ NOT

  


	NOT	SWITCH
NMOS	1um	1um
PMOS	2.91um	2.91um

❖ SWITCH

  


2-1. LOGIC GATE

 

□ Mosfet Width (Length = 100nm)


	2NOR	3NOR	4NOR	2NAND	3NAND	4NAND
NMOS	1um	1um	1um	1um	1um	1um
PMOS	3.99um	5um	5.96um	2.53um	2.31um	2.14um

 


2-2. MULTIPLEXER (MUX)

□ 2X1 MUX

❖ 2X1 MUX (Logic Gate)

 


❖ 2X1 MUX (Switch)

 


2-2. MULTIPLEXER (MUX)

❖ 2X1 MUX (Logic Gate)

 

❖ 2X1 MUX (Switch)

 

❖ 비교

2X1 MUX
(LOGIC GATE)


2X1 MUX
(SWITCH)

가로	5.02 nm	2.305 nm
----	---------	----------

세로	6.945 nm	7.035 nm
----	----------	----------


TR 개수	14	6
----------	----	---

2-2. MULTIPLEXER (MUX)

 


□ 4X1 MUX


❖ 4X1 MUX (Logic Gate)

 



❖ 4X1 MUX (Switch)

 

2-2. MULTIPLEXER (MUX)

 


❖ 4X1 MUX Simulation

  

2-2. MULTIPLEXER (MUX)


❖ 4X1 MUX (Logic Gate)

 

❖ 비교

4X1 MUX
(LOGIC GATE)

❖ 4X1 MUX (Switch)

 

4X1 MUX
(SWITCH)

가로

15.06 nm

6.2 nm

세로

6.945 nm



7.62 nm

TR 개수

42

16


2-3. ADDER

  


2-3. ADDER

□ Full Adder


❖ Schematic

 

❖ Layout


 


2-3. ADDER

 

□ Full Adder


❖ Full Adder Simulation

  


2-3. ADDER

□ 4-Bit Adder

❖ Schematic

 

❖ Layout

 


3. ANALOG CIRCUIT

Amplifier


Common Source (CS)
Amplifier

Differential
Amplifier

 

3-1. CS AMPLIFIER


❖ Schematic

 

❖ Simulation




❖ Layout

 


3-2. DIFFERENTIAL AMPLIFIER


❖ Schematic

 

❖ Simulation

 


❖ Layout

 




SUMMARY

 


 - ❖ Schematic and Layout flow
- ❖ How to reduce the size of circuit
- ❖ How to reduce the number of TR





CONTACT

 

E-mail

byoungjin@hanmail.net



Phone

010 2026 3457

