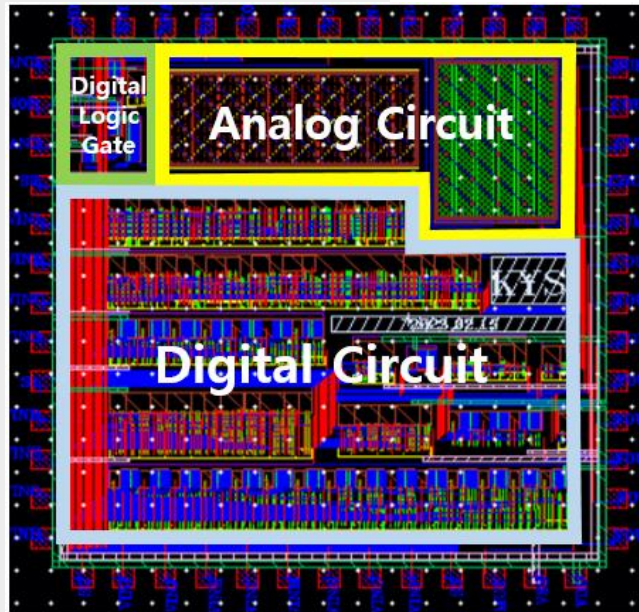


Cadence Full Custom IC

One Chip Design

Ph. D. ByoungJin Lee
byoungjin@hanmail.net
010 2026 3457

INDEX



01 Program & Tool

02 Digital Gates

PROGRAM & TOOLS

Cadence Virtuoso Schematic Editor / Layout Editor

Cadence Virtuoso Spectre / ADE

Assura(DRC & LVS)

GPDK090


DIGITAL CIRCUITS

Digital Logic Gates


- NOT / SWITCH / XOR
- 2NAND / 3NAND / 4NAND
- 2NOR / 3NOR / 4NOR

Digital Logic Gate – 2NAND


Schematic & Symbol

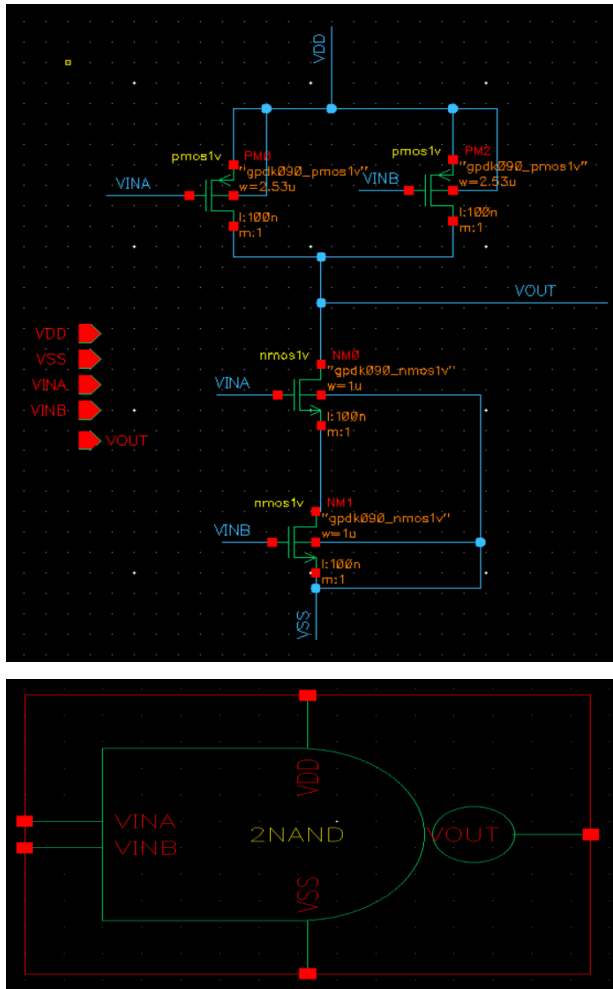

Layout


 


Simulation1


 


Digital Logic Gate - 2NAND

Simulation2

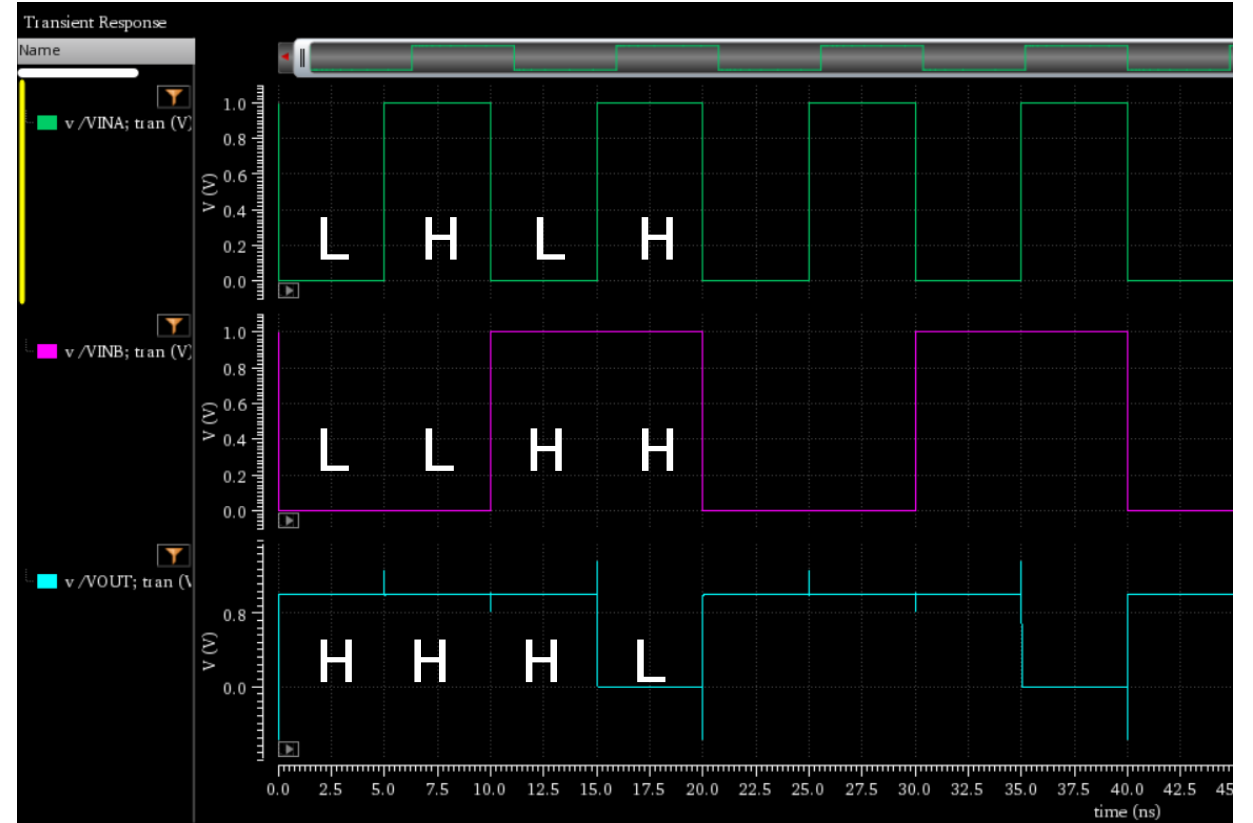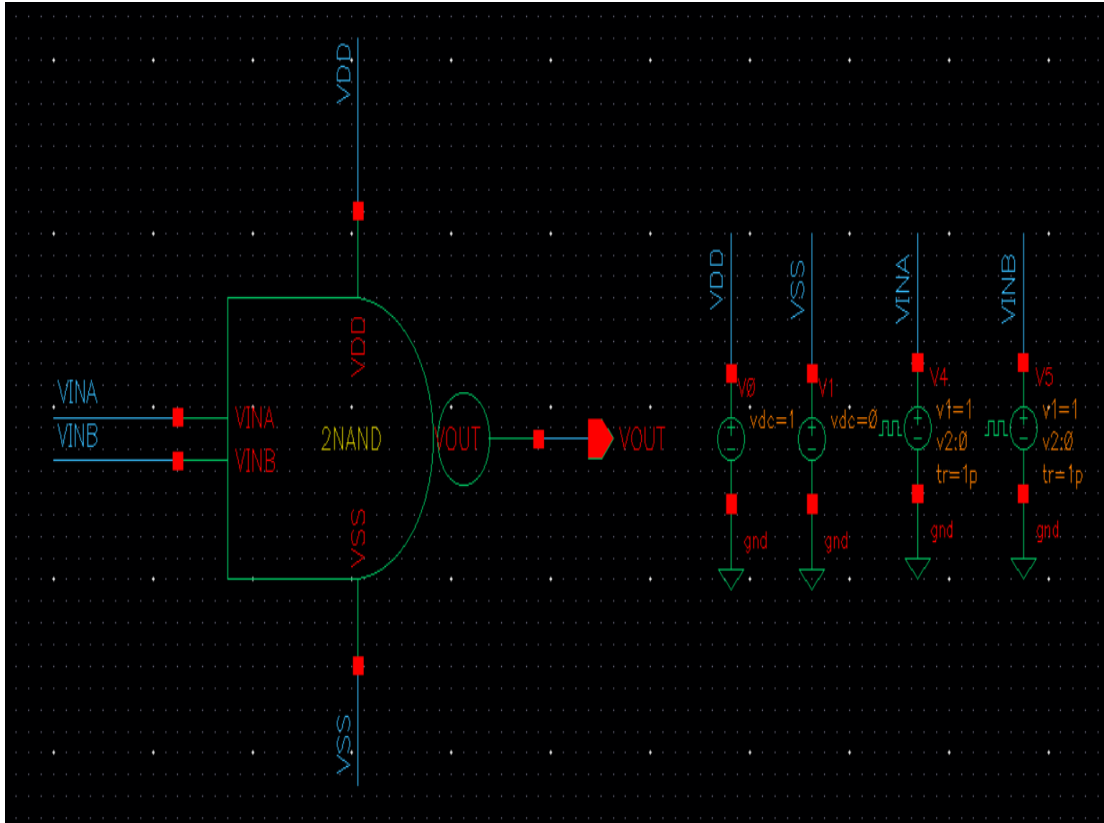


Digital Logic Gate - 2NAND

 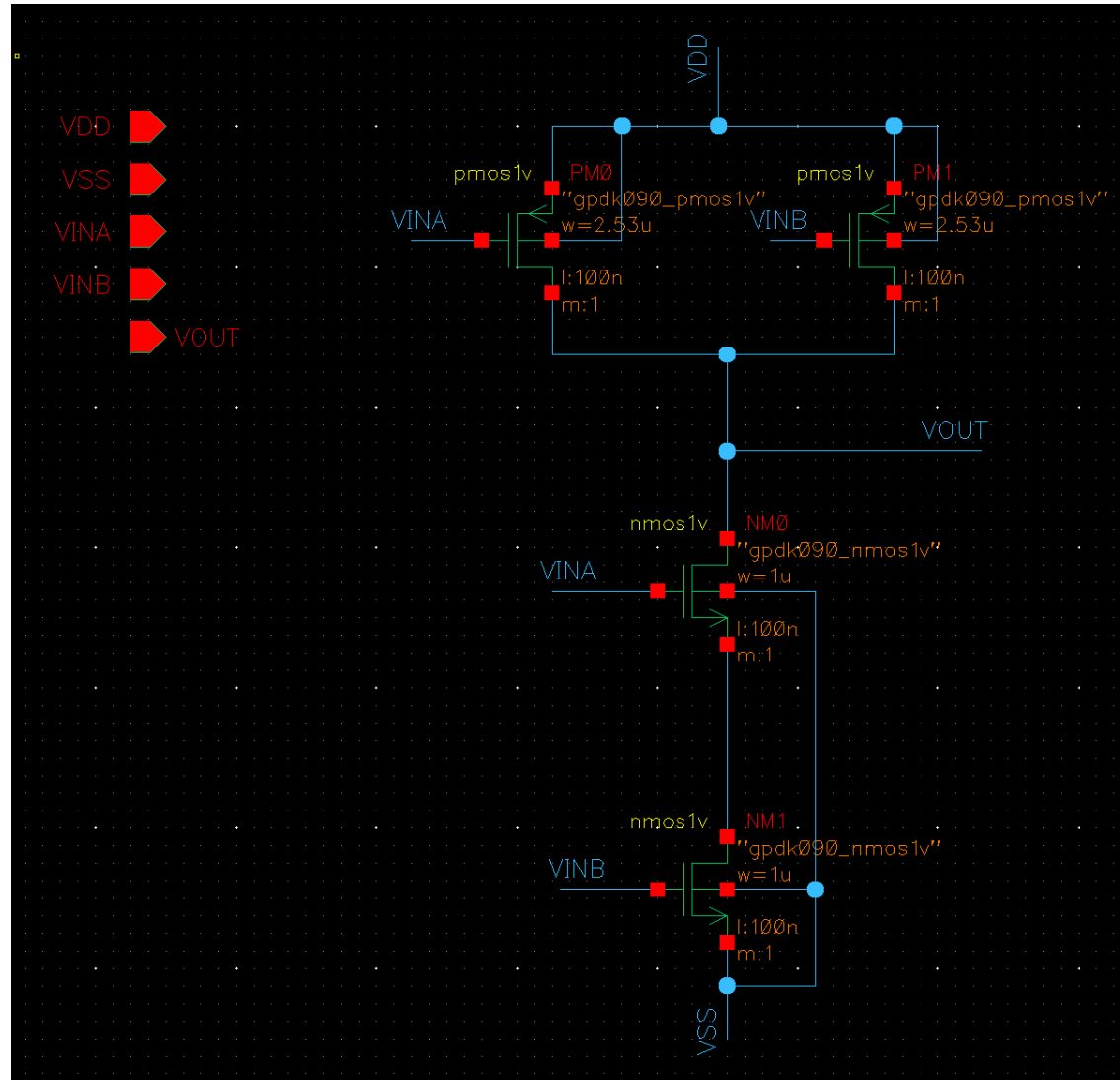


Digital Logic Gate – Schematic

Width	NOT	SWITCH	XOR	2NAND	3NAND	4NAND	2NOR	3NOR	4NOR
nMOS L=100nm	1um	1um	1um	1um	1um	1um	1um	1um	1um
pMOS L=100nm	2.91um	2.91um	2.91um	2.53um	2.31um	2.14um	3.99um	5um	5.96um

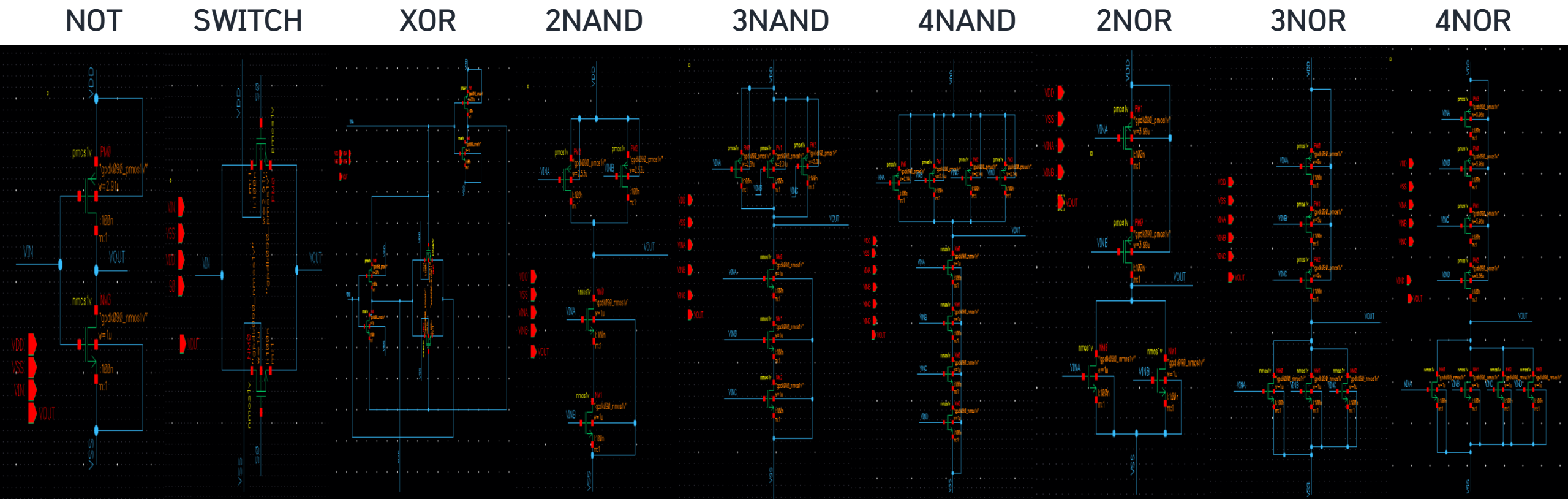


Digital Logic Gate – Layout

	NOT	SWITCH	2NAND	3NAND	4NAND	2NOR	3NOR	4NOR
Area (μm^2)	5.4802	5.6588	7.6160	10.0036	12.5180	9.6016	14.7918	20.9222

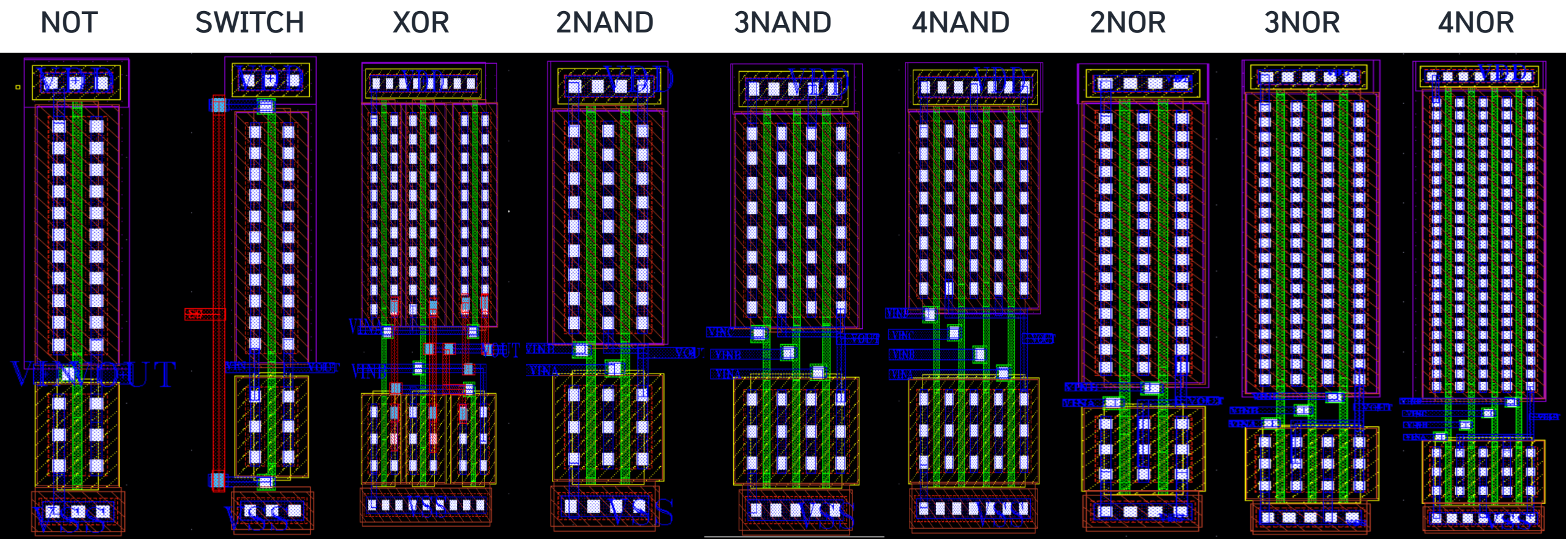


Digital Logic Gates

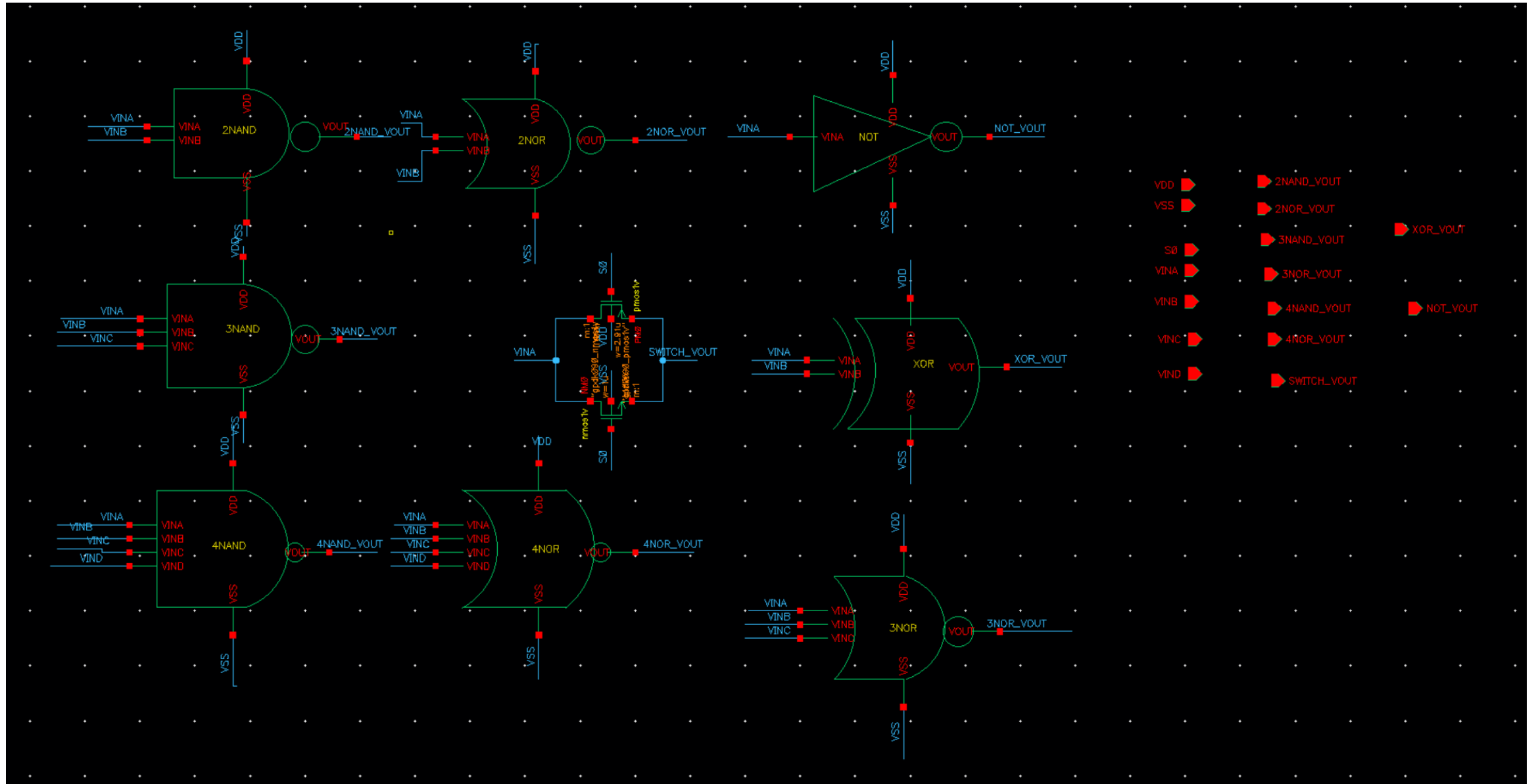

Digital Logic Gates

Group Layout

SIZE : 137.42um²

 

IMPLICATIONS

Price

Speed

Power

THANK YOU.

Ph. D. ByoungJin Lee
byoungjin@hanmail.net
010 2026 3457