



Cadence Full-Custom IC Design




# Common-Source Amplifier

---




Ph. D. ByoungJin Lee

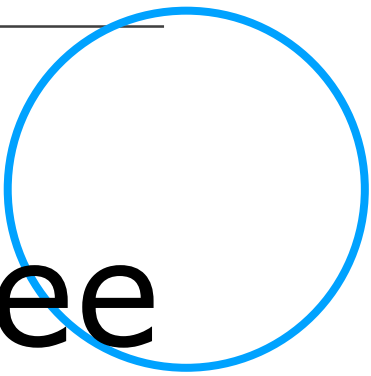





# INDEX

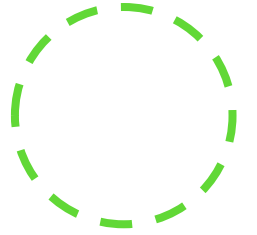


Program & Tool

Common-Source (CS) Amplifier

Theory / Schematic / Simulation / Layout / DRC/ LVS



One Chip

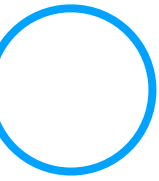





# PROGRAM & TOOL




Cadence Virtuoso Schematic Editor/Layout Editor

Cadence Virtuoso Spectre/ADE


Assura(LVS & DRC)

GPDK090

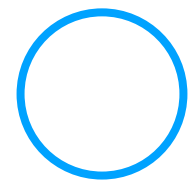




# The Common-Source (CS) Amplifier

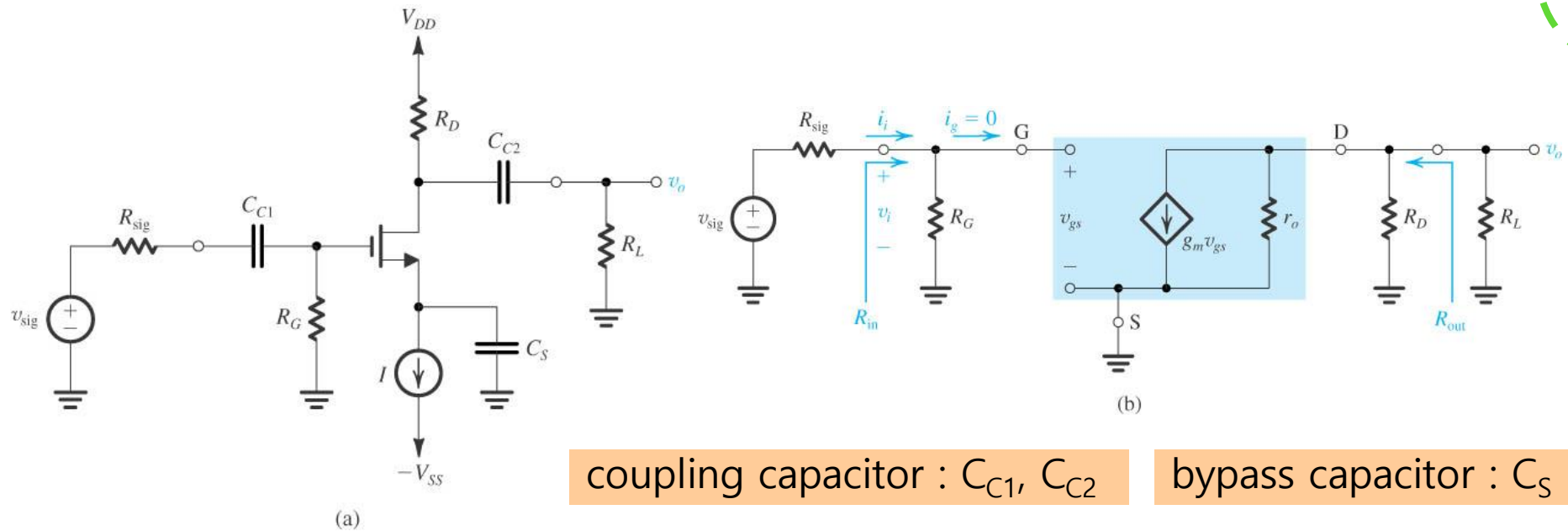

- ▶ input resistance :  $R_{in} = R_G$
- ▶ output resistance :  $R_{out} = r_o \parallel R_D$
- ▶ voltage gain :  $A_v = -g_m (r_o \parallel R_D \parallel R_L)$
- ▶ overall voltage gain :  $G_v = -\frac{R_G}{R_G + R_{sig}} g_m (r_o \parallel R_D \parallel R_L)$
- ▶ applications : part of a larger amplifier circuit



# Directly on the Circuit

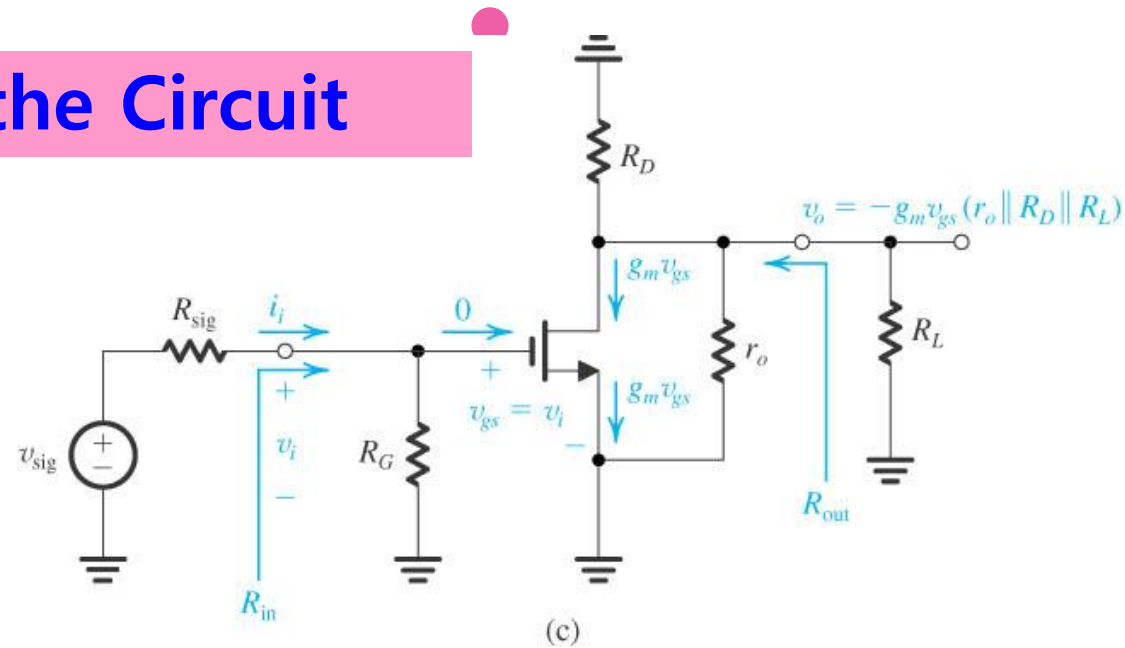

$$\frac{v_i}{v_{sig}} = \frac{R_{in}}{R_{sig} + R_{in}} = \frac{R_G}{R_{sig} + R_G}$$

$$G_m \equiv \left. \frac{i_o}{v_i} \right|_{R_L=0} = -g_m \quad R_{outtotal} = r_o \parallel R_D \parallel R_L$$



$$A_v = \frac{v_o}{v_i} = G_m R_{outtotal} = -g_m (r_o \parallel R_D \parallel R_L)$$

$$G_v = \frac{v_o}{v_{sig}} = \frac{v_i}{v_{sig}} \frac{v_o}{v_i} = -\frac{R_G}{R_G + R_{sig}} g_m (r_o \parallel R_D \parallel R_L)$$



# The Common-Source Amplifier with a Source Resistance

neglecting  $r_o$

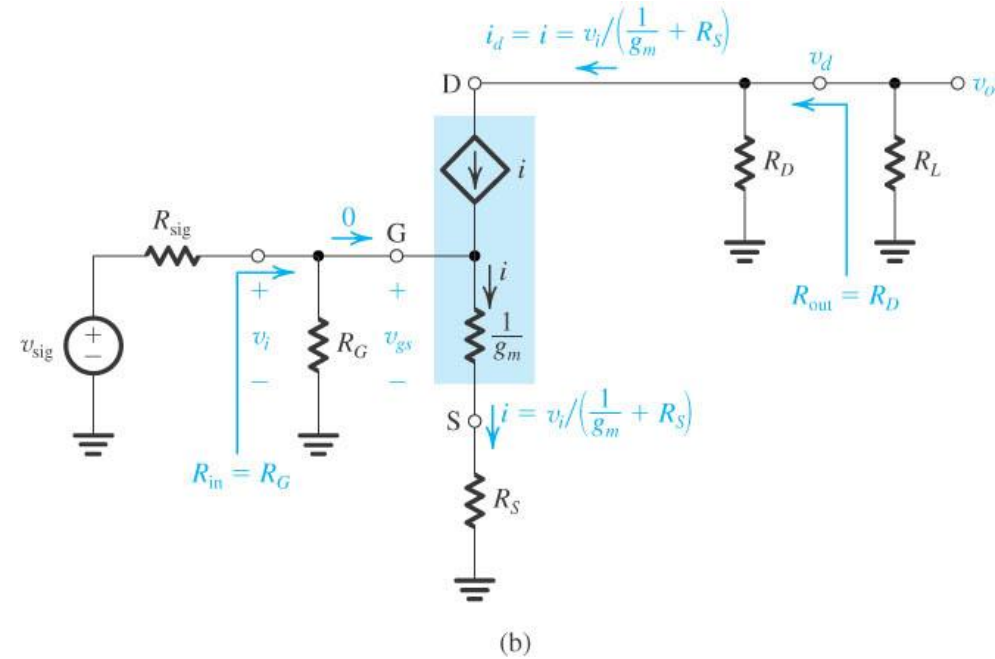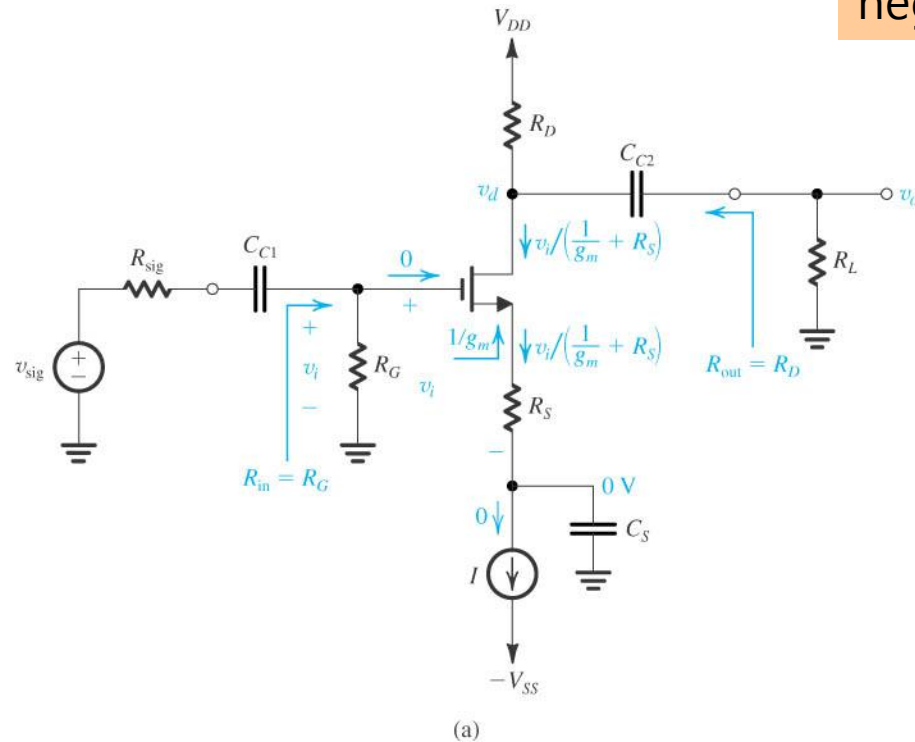

- ▶ input resistance :  $R_{in} = R_G$
- ▶ output resistance :  $R_{out} = R_D$





► voltage gain :

$$v_{gs} = \frac{1/g_m}{(1/g_m) + R_S} v_i = \frac{v_i}{1 + g_m R_S}$$


$$i_d = i = \frac{v_i}{(1/g_m) + R_S} = \frac{g_m v_i}{1 + g_m R_S}$$

$$v_o = -i_d (R_D \parallel R_L) = -\frac{g_m (R_D \parallel R_L)}{1 + g_m R_S} v_i$$

$$A_v = -\frac{g_m (R_D \parallel R_L)}{1 + g_m R_S}$$

► overall voltage gain :  $G_v = -\frac{R_G}{R_G + R_{sig}} \frac{g_m (R_D \parallel R_L)}{1 + g_m R_S}$

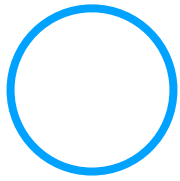► source degeneration resistor  $R_S$  : reduction of the gain by  $(1 + g_m R_S)$





## Directly on the Circuit

$$v_i = v_{gs} + R_S i_d = i_d / g_m + R_S i_d = (1 / g_m + R_S) i_d$$

$$G_m \equiv \left. \frac{i_o}{v_i} \right|_{R_L=0} = -\frac{i_d}{v_i} = -\frac{1}{1 / g_m + R_S}$$

$$R_{outtotal} = R_D // R_L$$


$$A_v = G_m R_{outtotal} = -\frac{R_D // R_L}{1 / g_m + R_S} = -\frac{g_m (R_D // R_L)}{1 + g_m R_S}$$

► useful interpretation :

$$A_v = -\frac{\text{total resistance in the drain}}{\text{total resistance in the source}} = -\frac{R_D // R_L}{1 / g_m + R_S}$$



# MOSFET SIMULATION SETUP

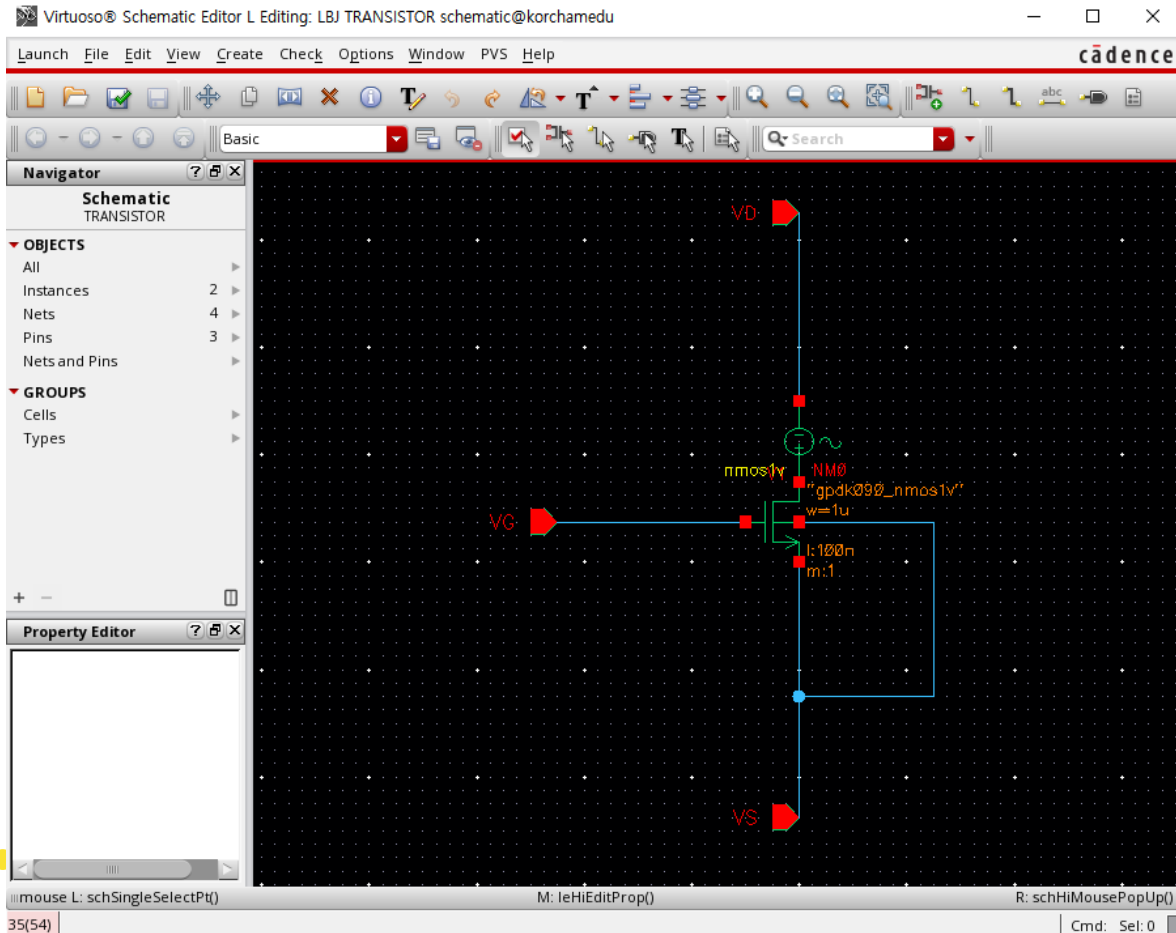

MOSFET	Length( $\mu\text{m}$ )	Fingers	Finger Width( $\mu\text{m}$ )	Total Width( $\mu\text{m}$ )
NMOS(NM0)	0.1	1	1	1



Virtuoso® Schematic Editor L Editing: LBJ TRANSISTOR\_TEST schematic@korchamedu

Launch File Edit View Create Check Options Window PVS Help

Basic

Launch

- ADE L
- ADE XL
- ADE GXL
- ADE Explorer
- ADE Assembler
- Layout XL
- Layout GXL
- Layout EAD
- Schematics L
- Schematics XL

Property Editor


mouse L: schSingleSelectPt()

37(56) ADE L


M: leHiEditProp()

R: schHiMousePop()

Cmd: Sel:

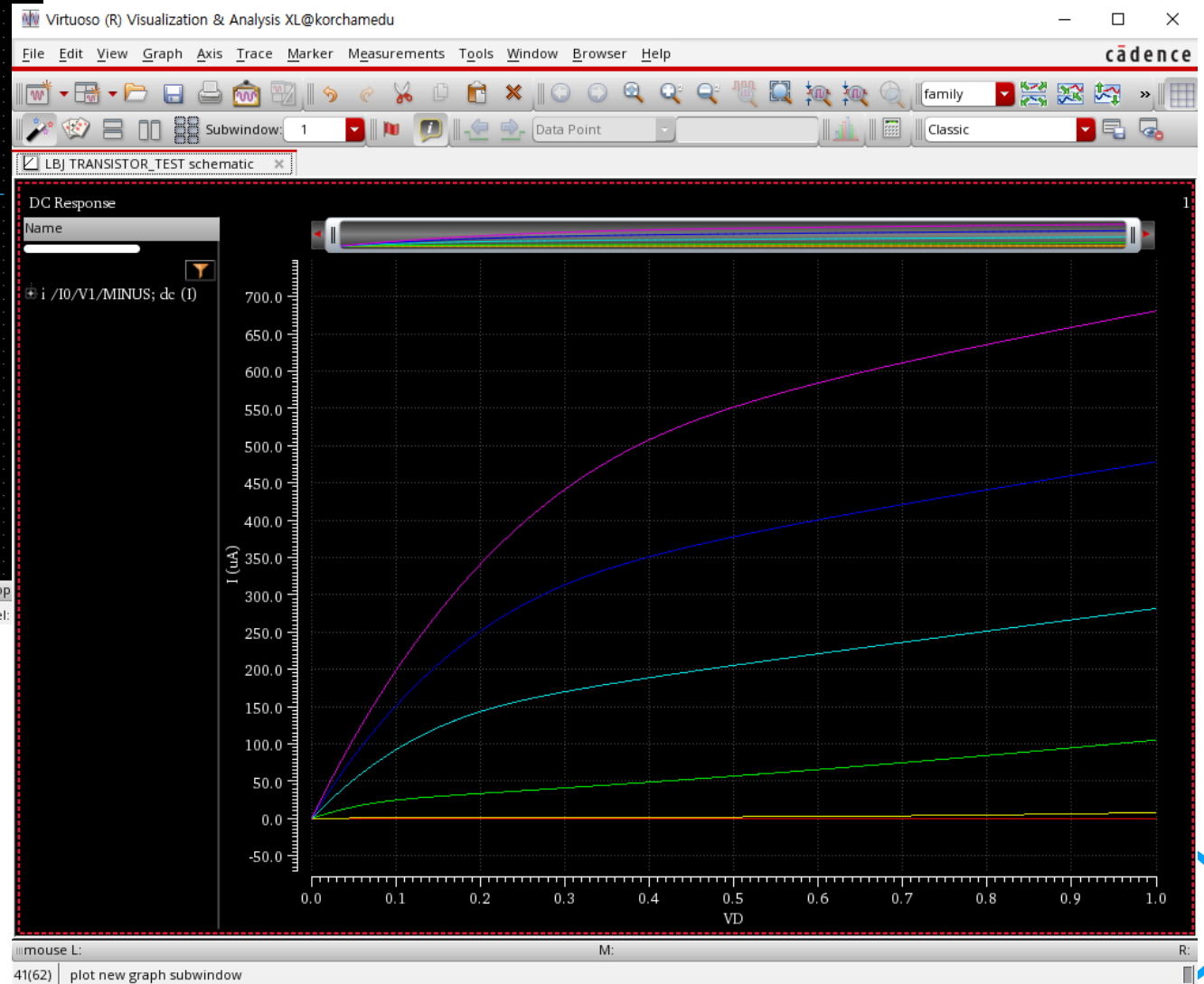









# CS AMP SIMULATION SETUP

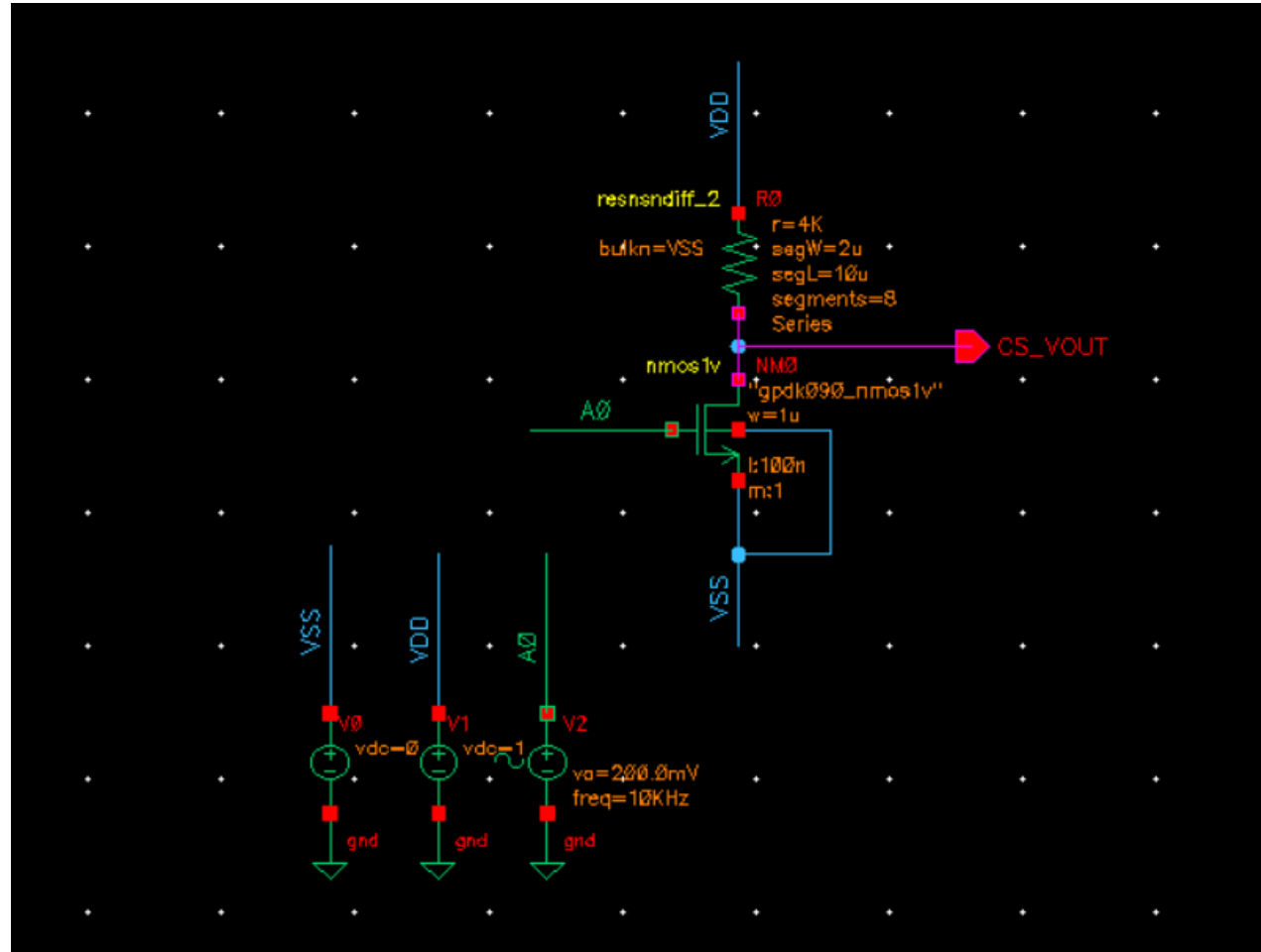





# VOLTAGE GAIN

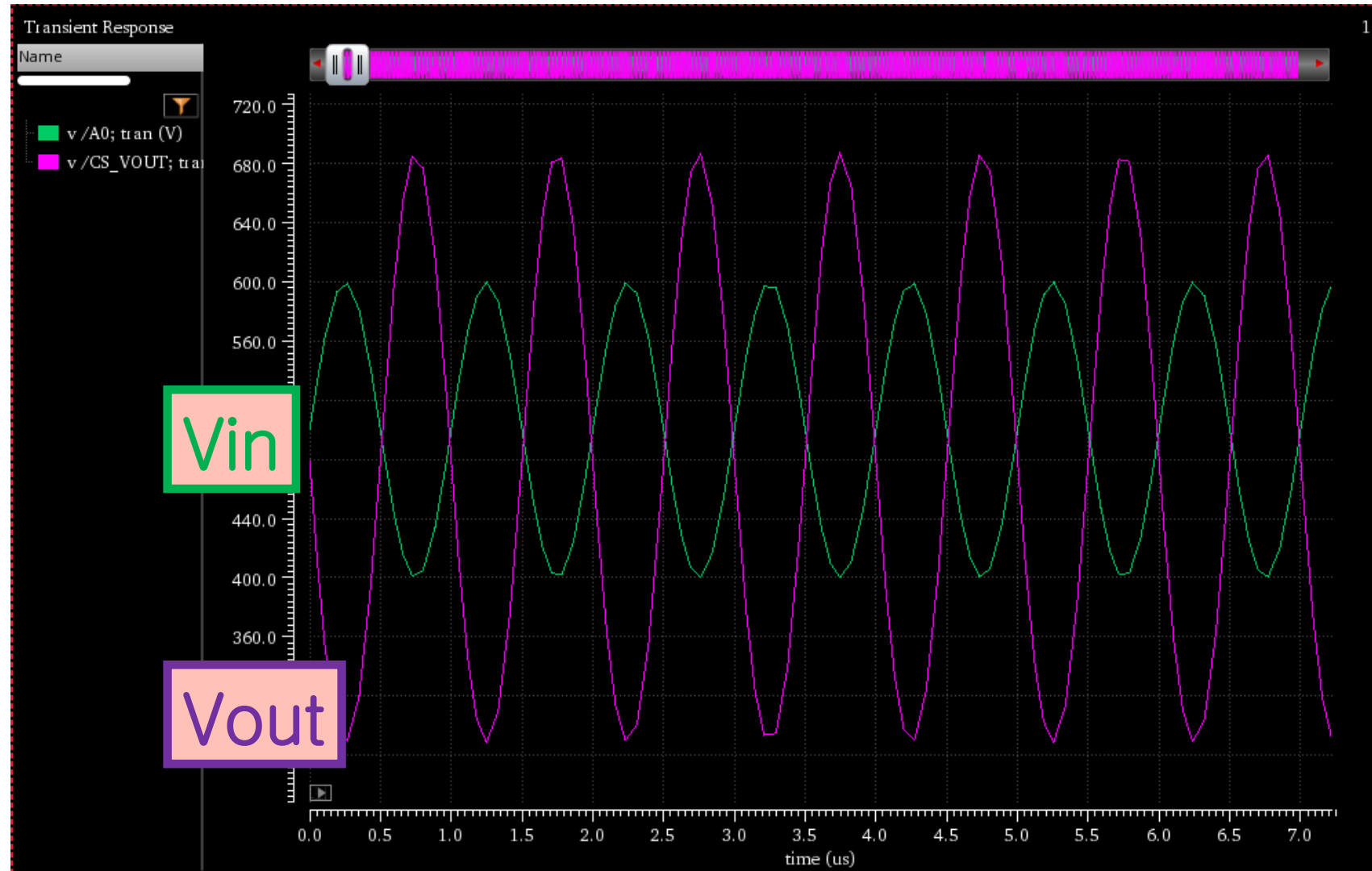




# 20dB & Phase

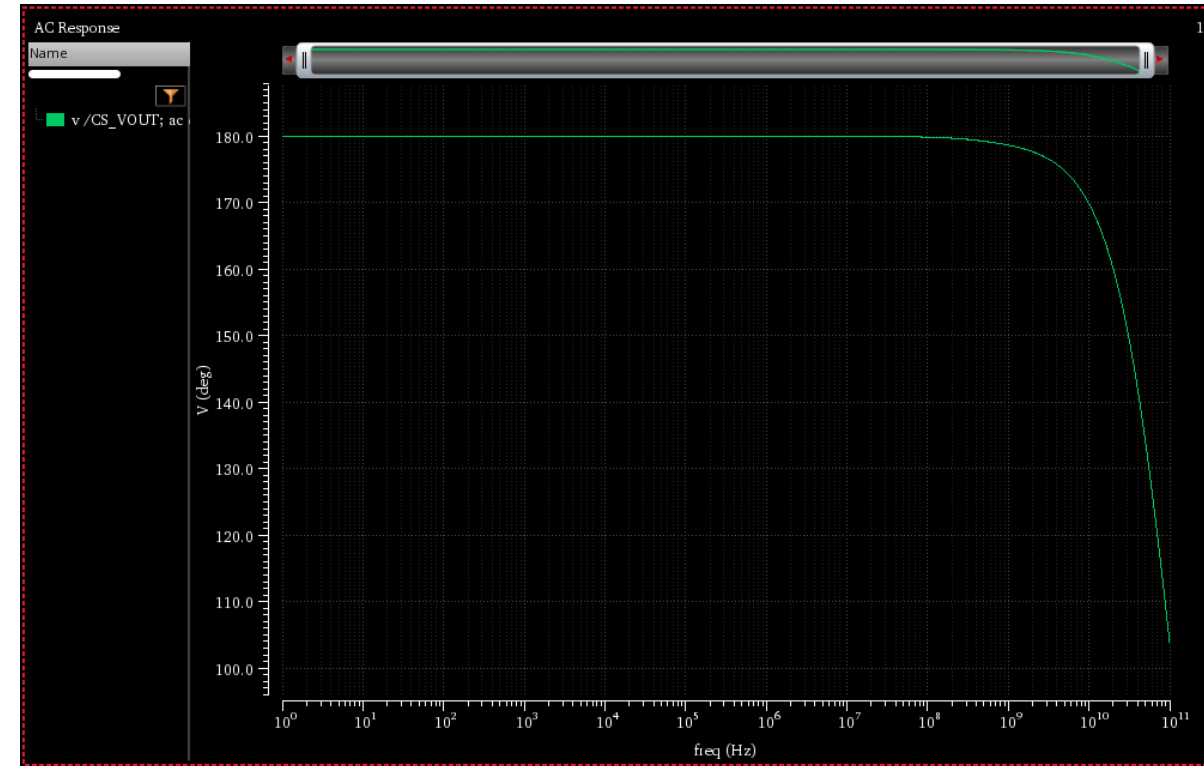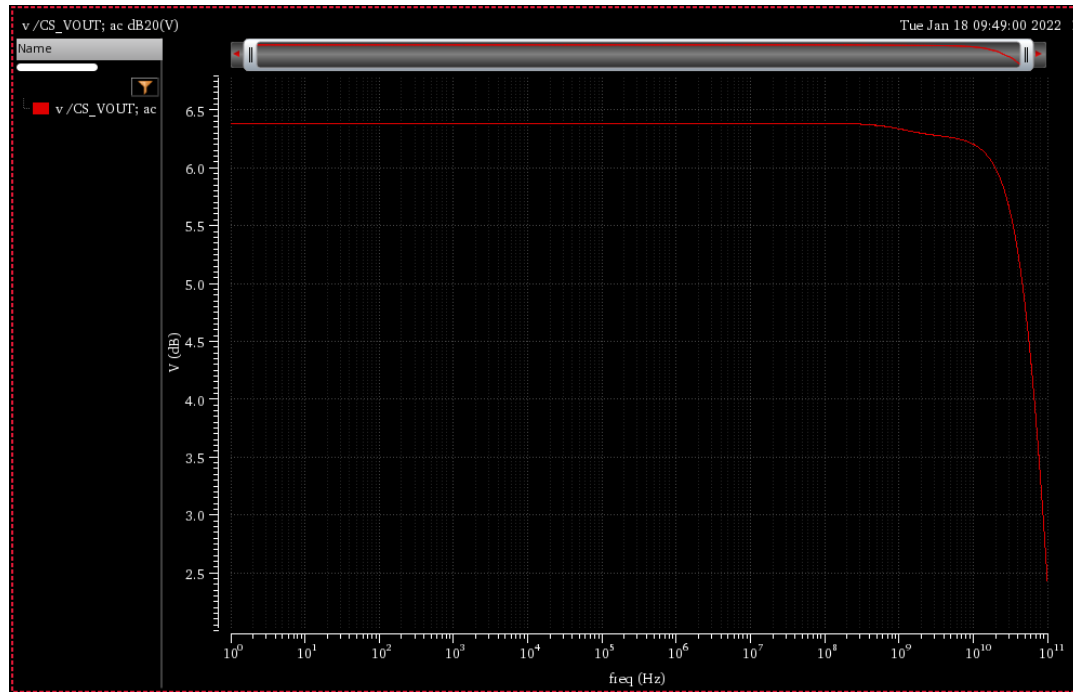



# CS AMP LAYOUT SETUP

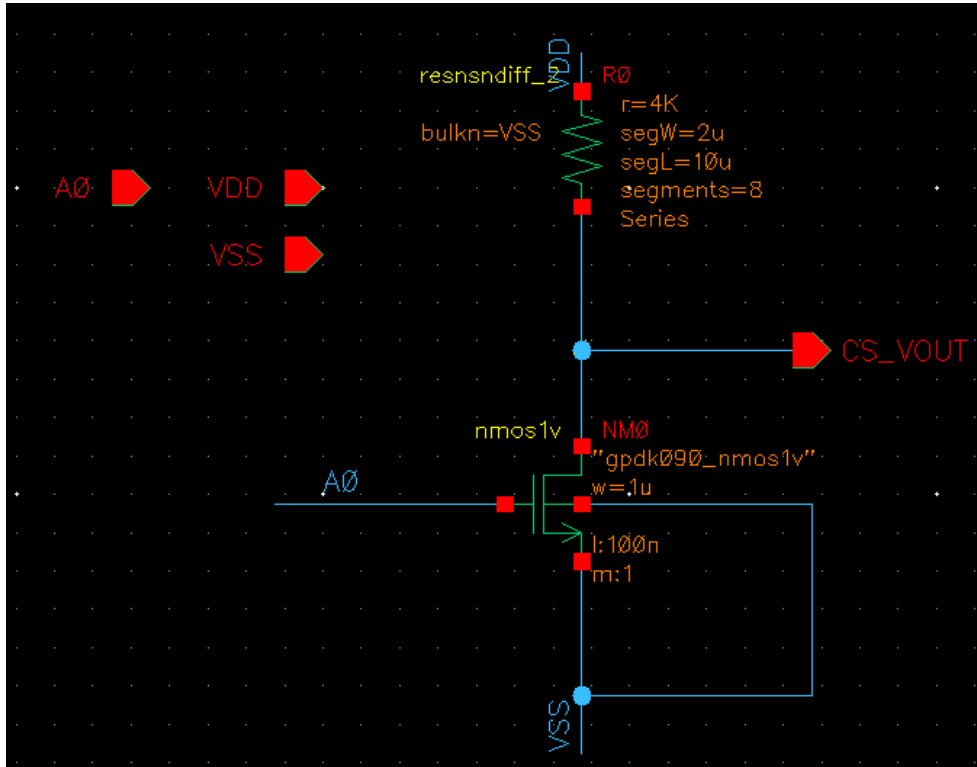


Component	MOSFET	Component	Resistor
Type	nmos1v	Type	resnapdiff_2
Length	100nm	Width( $\mu\text{m}$ )	2
Finger	1	No. of Segments	8
Finger Width( $\mu\text{m}$ )	1	Segment Length( $\mu\text{m}$ )	10
Total Width( $\mu\text{m}$ )	1	Total Length( $\mu\text{m}$ )	80
		Total Resistance	4k $\Omega$






# CS AMP LAYOUT

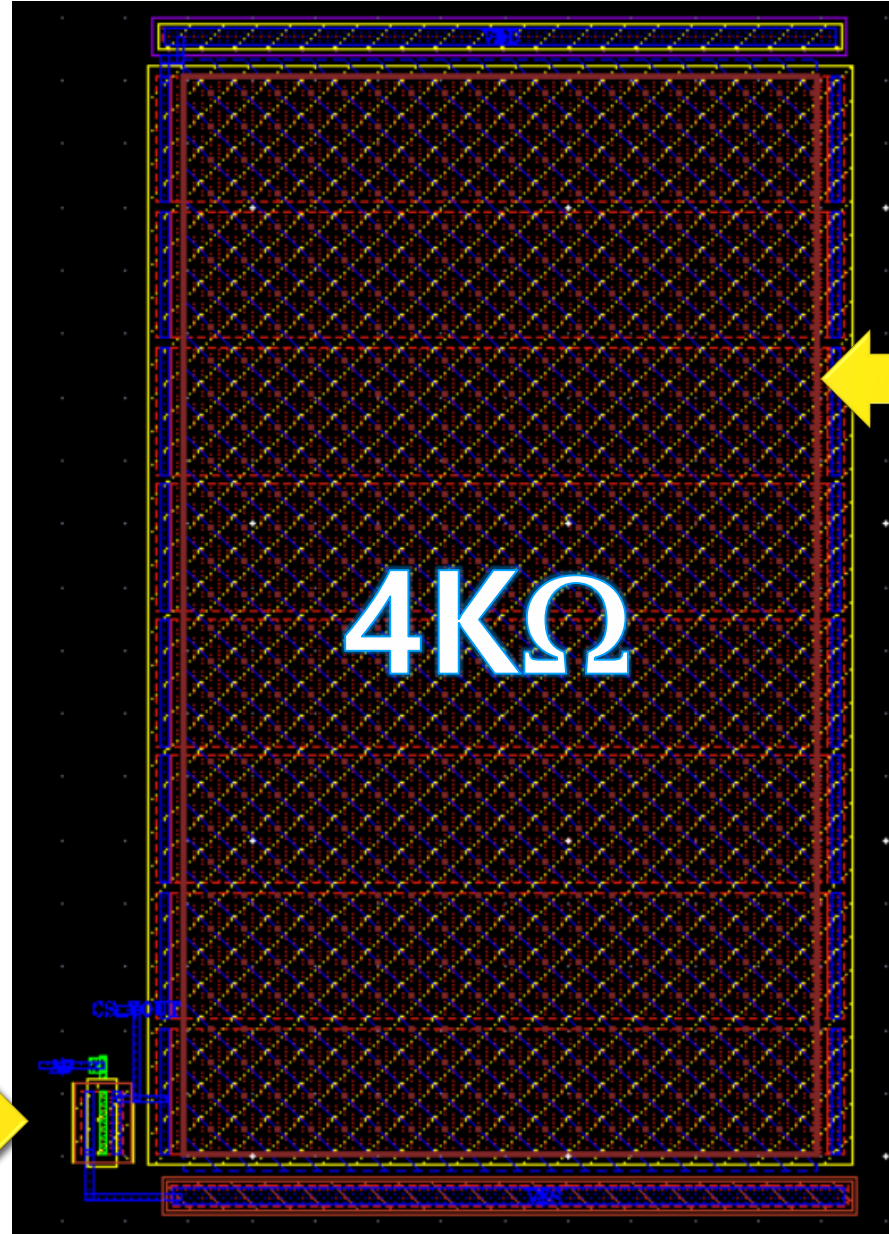

RESISTOR

TRANSISTOR

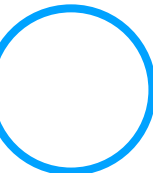



# CS AMP (DRC)

Run Assura DRC@korchamedu

Layout Design Source: DFI ☐ Compare two layouts ☐ Generate Lvl. Compare Rules...

Library: SSH Cell: CS\_AMP View: layout Browse...

Save Extracted View ☐ View Name: drc\_extracted

Area To Be Checked: Full

Run Name: CS\_AMP Run Directory: ./DRC

Run Location: local

View Rules Files ☒ Technology: -undefined- Rule Set: default

Rules File: ./assura/drc.ru1 View... Edit.. Reload

Switch Names: Set Switches

RSF Include: View... Edit..


Variable	Value	Default	Description
None			

View avParameters ☐ Modify avParameters... 1 avParameter is set.

View Additional Functions ☐ No additional functions are set.




Enable limitDrcCheck ☐

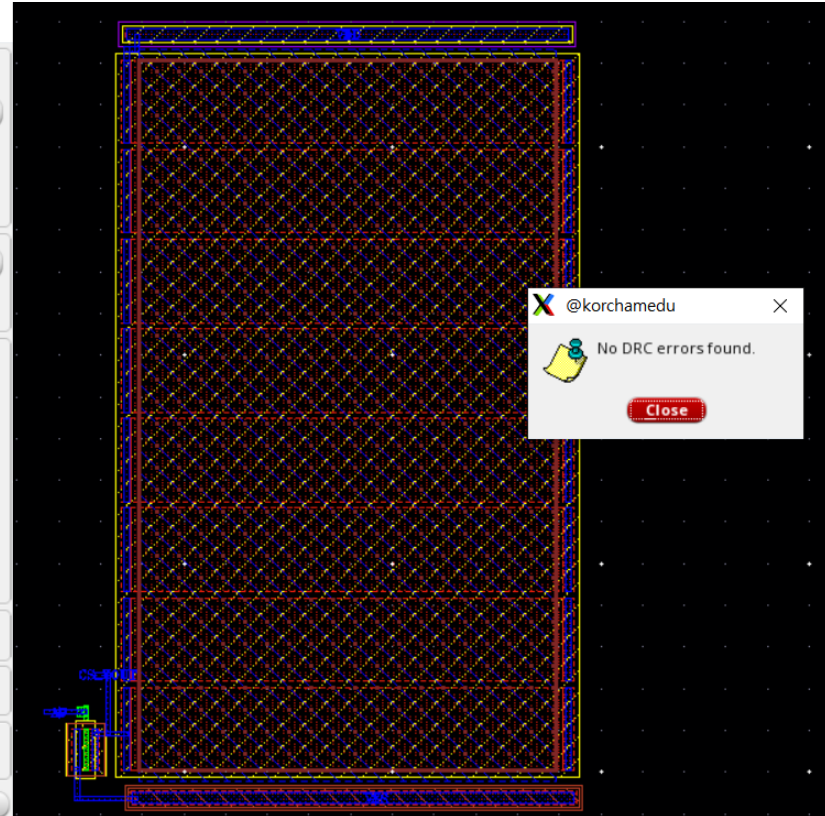OK Cancel Apply Defaults Load State Save State View RSF Help






# CS AMP (LVS)

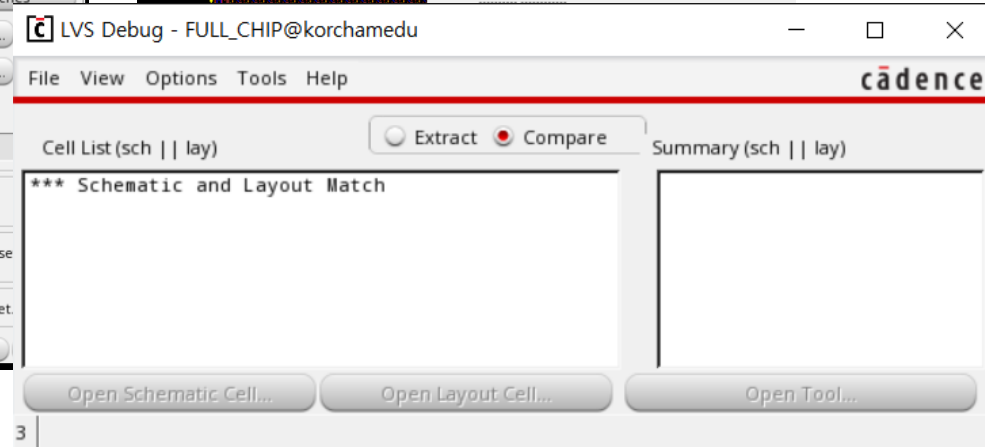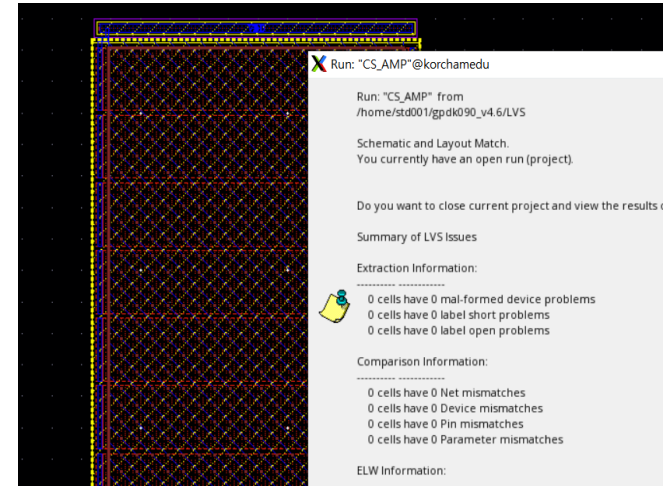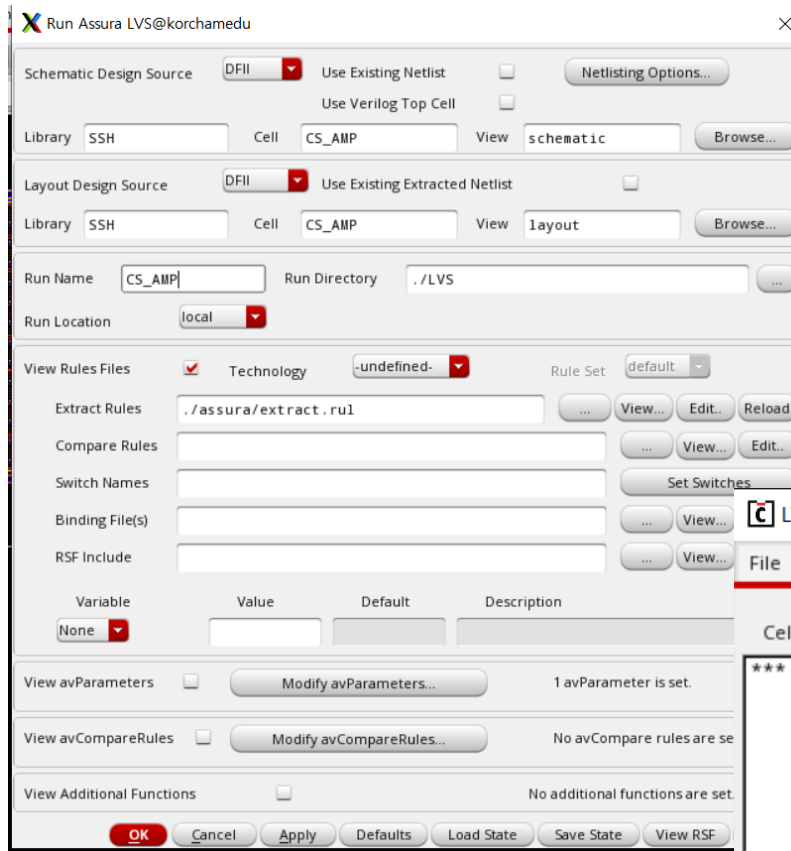





# CONTACT

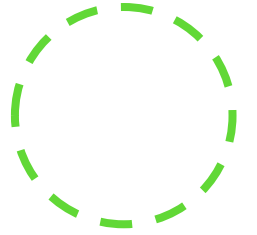

## **E-mail**

byoungjin@hanmail.net



## **Phone**

010 2026 3457

